

# Digital to Analog Converter

A way to explore Op-amps and GPIO


# The Point of DAC

- Substantial and growing digital interface to analog world
- Two directions of conversion:
  - ADC: analog to digital converter
    - more common; analog input to computer
    - sensors of all types produce voltage proportional to quantity of interest
  - DAC: digital to analog converter
    - so computer can create analog output (voltage)
    - more fundamental; at core of ADC in guess-and-check scheme

# Bit Level

- We'll do 8-bit DAC
  - 256 values; considered pretty crude
  - roughly 20 mV steps if 5-volt range
- 10 bit: 1,024 values; still at low end
- 12-bit: 4,096 values; often a reasonable choice
  - like the ADS1015 unit we used for RTD work
- 14-bit: 16,384 values; seldom need more
  - 0.3 mV resolution at 5 V starts to strain meaningfulness
- 16-bit: 65,536; high-end
  - 75  $\mu$ V resolution at 5 V; fairly common as 16 bits convenient
  - but often least significant bits lack practical meaning

# 8-bit DAC Concept: Current Summing

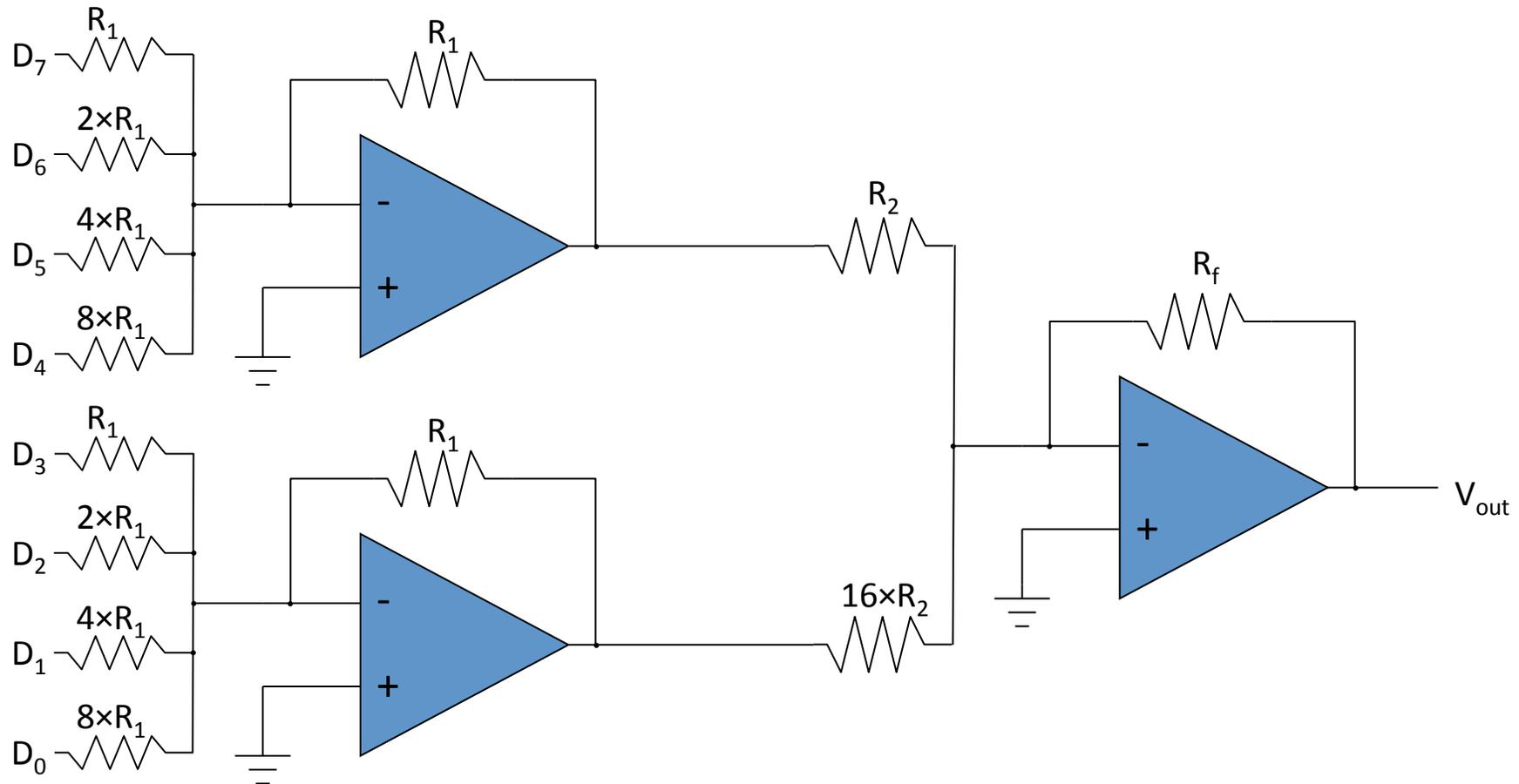


- Factors of 2 in identical 4-bit "nibble" stages
- Factor of 16 in second stage
- Same voltage (or zero) at each  $D_n$  input (digital)
  - voltage at intermediate nodes multiple of  $-V_{\text{digital}}/8$  times integer 0–15
- Can tune final  $R_f$  to achieve desired scale

# Cleaning Up Noisy Digital Input

- The  $D_0\dots D_7$  inputs should all be the same voltage, and a known/reliable one
- But digital output from the Pi is not guaranteed to be steady or even the same from one pin to the next
- Want a way to use digital input to “switch-in” a clean reference
- Enter the MOSFET

# Input Circuit Preview

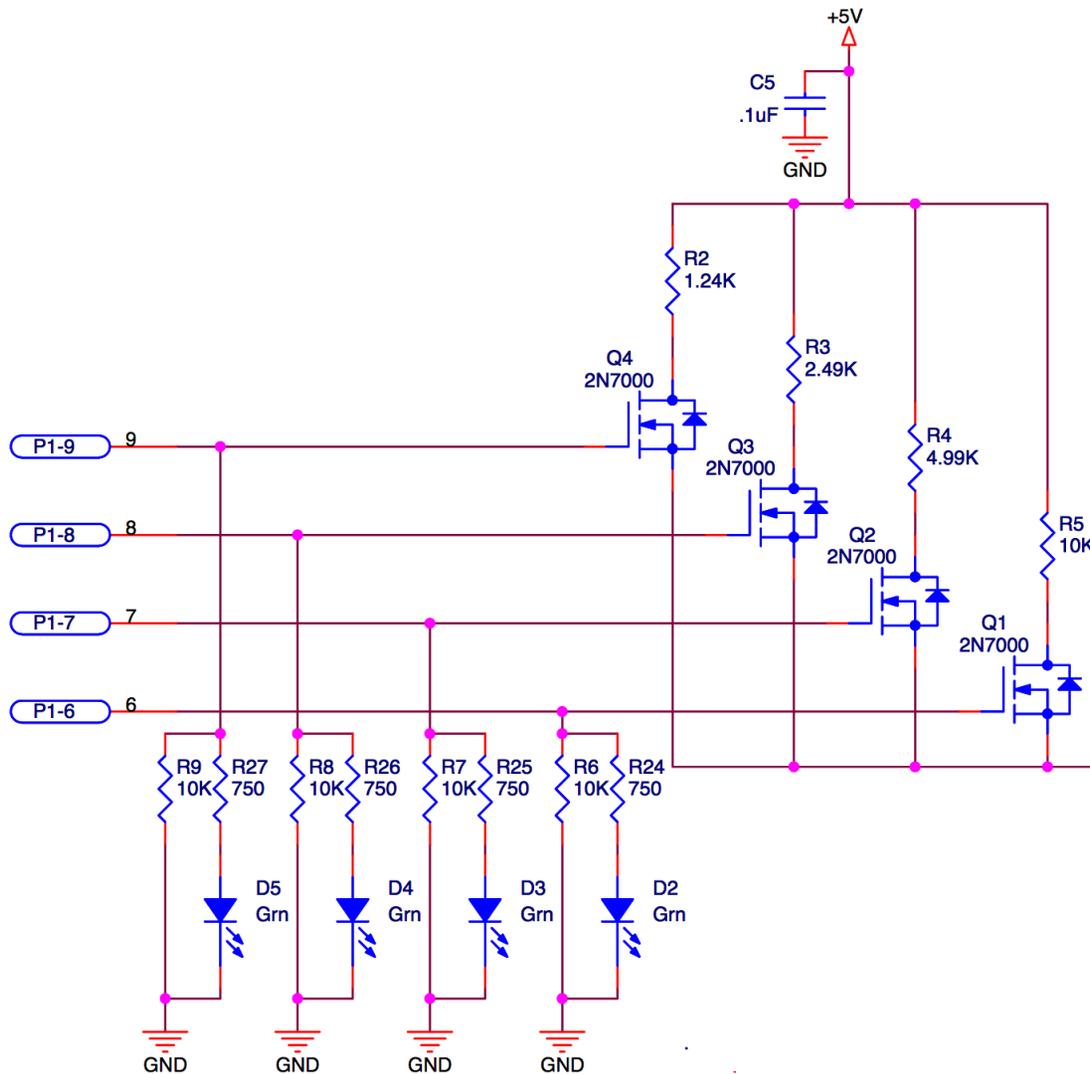

- 5V reference at top
- 4-bits of input control MOSFETs
- Note 1:2:4:8 resistors
- 10k resistors pull down to ground when digital zero
- LED & limiter indicate ON

# Field-Effect Transistors


- The “standard” npn and pnp transistors use **base-current** to control the transistor current
- FETs use a field (**voltage**) to control current
- Result is **no current flows** into the control “gate”
- FETs are used almost exclusively as switches
  - pop a few volts on the control gate, and the effective resistance is nearly zero

2N7000 FET


ON CHARACTERISTICS*						
$V_{GS(th)}$	Gate Threshold Voltage	$V_{DS} = V_{GS}, I_D = 1 \text{ mA}$	0.8	2.1	3	V
$r_{DS(on)}$	Static Drain-Source On-Resistance	$V_{GS} = 10\text{V}, I_D = 0.5\text{A}$ $T_C = 125^\circ\text{C}$		1.2	5	$\Omega$
				1.9	9	$\Omega$
$V_{DS(on)}$	Drain-Source On-Voltage	$V_{GS} = 10\text{V}, I_D = 0.5\text{A}$		0.6	2.5	V
		$V_{GS} = 4.5\text{V}, I_D = 75 \text{ mA}$		0.14	0.4	V
$I_{D(on)}$	On-State Drain Current	$V_{GS} = 4.5\text{V}, V_{DS} = 10\text{V}$	75	600		mA
$g_{FS}$	Forward Transconductance	$V_{DS} = 10\text{V}, I_D = 200 \text{ mA}$	100	320		ms

# FET Generalities

FET

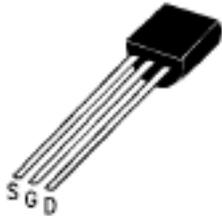

BJT

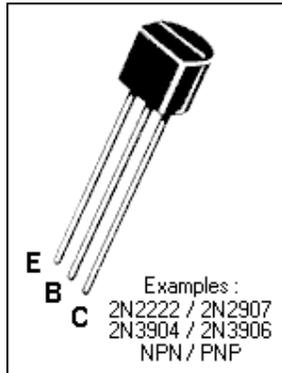


note pinout  
correspondence

- Every FET has at least three connections:
  - source (S)
    - akin to emitter (E) on BJT
  - drain (D)
    - akin to collector (C) on BJT
  - gate (G)
    - akin to base (B) on BJT
- Some have a body connection too
  - though often tied to source


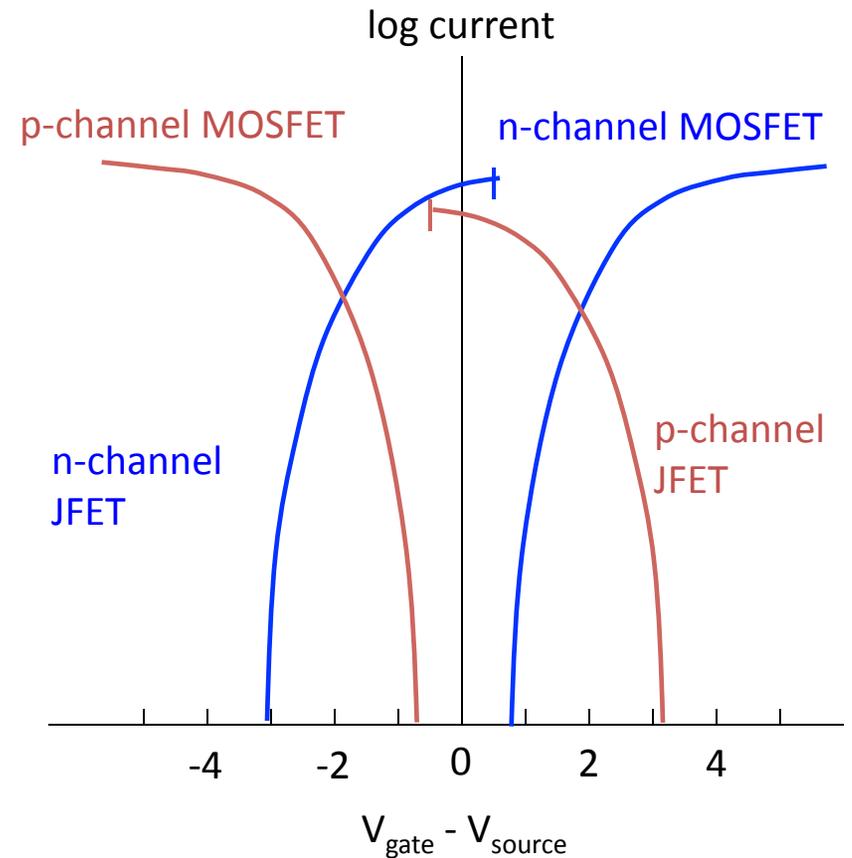
# FET Types

- Two flavors: **n** and **p**
- Two types: JFET, MOSFET
- MOSFETs more common
- JFETs conduct “by default”
  - when  $V_{\text{gate}} = V_{\text{source}}$
- MOSFETs are “open” by default
  - must turn on deliberately
- JFETs have a p-n junction at the gate, so must not forward bias more than 0.6 V
- MOSFETs have total isolation: do what you want



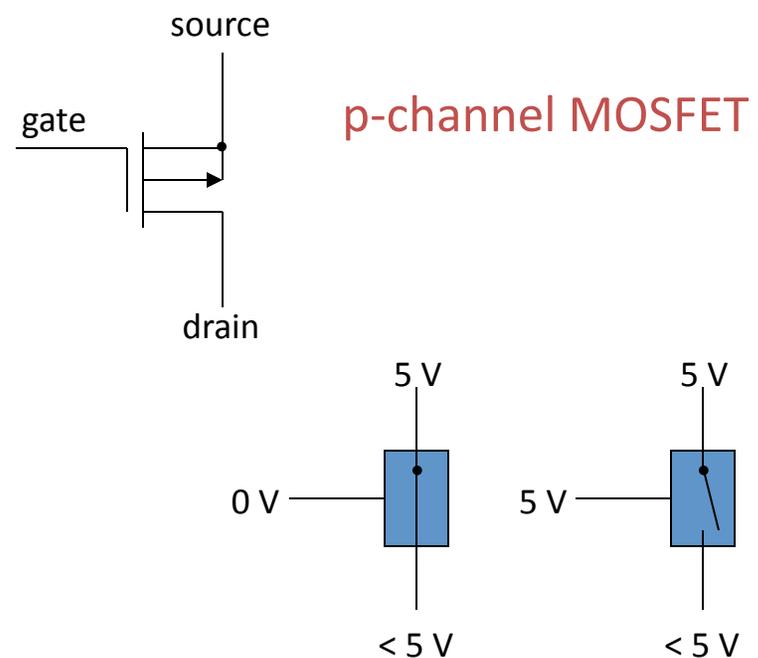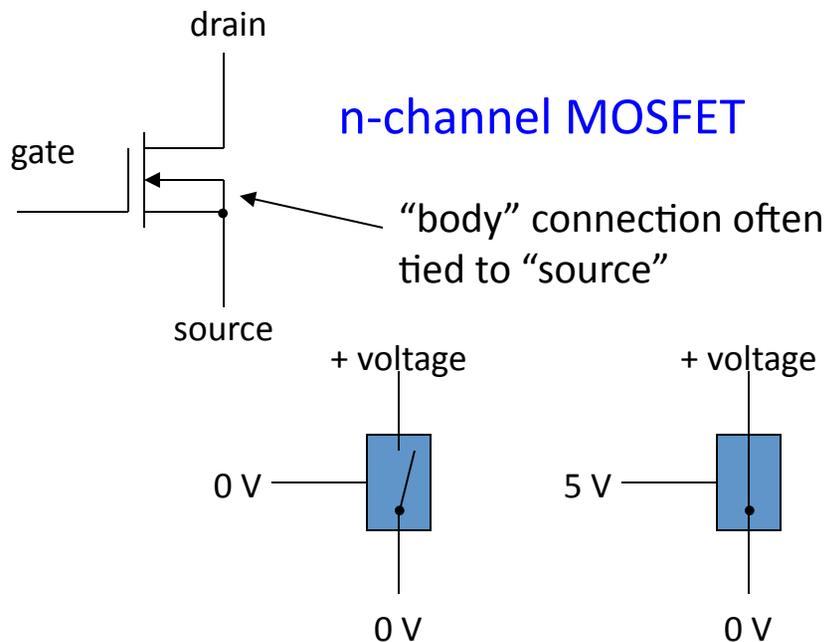
# MOSFET Switches

- MOSFETs, as applied to logic designs, act as **voltage-controlled switches**
  - **n-channel** MOSFET is closed (conducts) when positive voltage (+5 V) is applied, open when zero voltage
  - **p-channel** MOSFET is open when positive voltage (+5 V) is applied, closed (conducts) when zero voltage
    - (MOSFET means metal-oxide semiconductor field effect transistor)



# Input Circuit Revisited

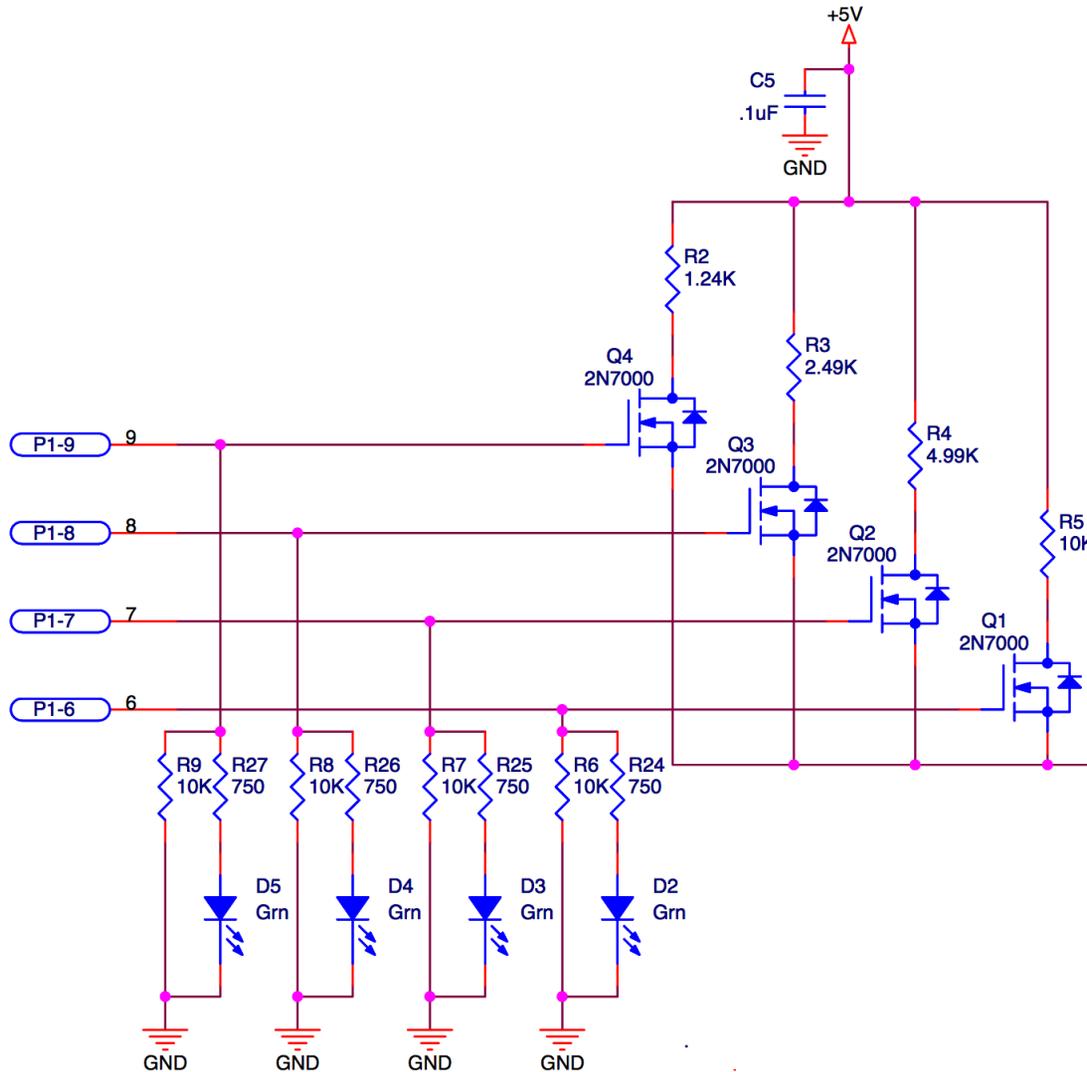

- 5V reference at top
- Digital LOW on gate has MOSFET OFF
  - no current
  - drain at 5V
- Digital HIGH makes MOSFET like a short
  - current flows (to op-amp summing junction)
  - drain will be near ground
- 3.3 V from GPIO plenty to switch MOSFETs

# Lab 7a

- Build 8-bit input stage and DAC on breadboard and verify operation
  - hits expected target values given input bit pattern
- Ready for Lab 7b; flinging digital data from the Raspberry Pi

## Raspberry Pi 4 B J8 GPIO Header

Pin#	NAME		NAME	Pin#
01	3.3v DC Power		DC Power 5v	02
03	GPIO02 (SDA1, I <sup>2</sup> C)		DC Power 5v	04
05	GPIO03 (SCL1, I <sup>2</sup> C)		Ground	06
07	GPIO04 (GPCLK0)		(TXD0, UART) GPIO14	08
09	Ground		(RXD0, UART) GPIO15	10
11	GPIO17		(PWM0) GPIO18	12
13	GPIO27		Ground	14
15	GPIO22		GPIO23	16
17	3.3v DC Power		GPIO24	18
19	GPIO10 (SPI0_MOSI)		Ground	20
21	GPIO09 (SPI0_MISO)		GPIO25	22
23	GPIO11 (SPI0_CLK)		(SPI0_CE0_N) GPIO08	24
25	Ground		(SPI0_CE1_N) GPIO07	26
27	GPIO00 (SDA0, I <sup>2</sup> C)		(SCL0, I <sup>2</sup> C) GPIO01	28
29	GPIO05		Ground	30
31	GPIO06		(PWM0) GPIO12	32
33	GPIO13 (PWM1)		Ground	34
35	GPIO19		GPIO16	36
37	GPIO26		GPIO20	38
39	Ground		GPIO21	40

## Raspberry Pi 4 B J14 PoE Header

01	TR01		TR00	02
03	TR03		TR02	04

## Pinout Grouping Legend

Inter-Integrated Circuit Serial Bus		Serial Peripheral Interface Bus	
Ungrouped/Un-Allocated GPIO		Universal Asynchronous Receiver-Transmitter	
Reserved for EEPROM			

# RPi Interface

- 40-pin header on side of RPi
- serial is orange (UART)
- I<sup>2</sup>C is light blue
- SPI is purple
- GPIO is green
  - and can also use any pin labeled GPIOxx

# GPIO on the Raspberry Pi

- 28 pins labeled GPIO00 to GPIO27
  - even those designated for SPI, I<sup>2</sup>C, UART fair game
  - just not the 12 power and ground pins!
- Numbering scheme is called BCM
  - Broadcom SOC (system on chip)
  - adheres to native numbering of Broadcom CPU used in Pi
  - does not follow 40-pin header numbering; skips around
- Digital values on 3.3 V standard
- Low-level C programs can switch at > 20 MHz
- Python native library switches around 70 kHz
  - see <https://codeandlife.com/2012/07/03/benchmarking-raspberry-pi-gpio-speed/>

# Python Interface

- Library called RPi.GPIO installed (by default) on Pi
- Example; toggle pin 40 (GPIO21)

```
import RPi.GPIO as GPIO      # rename for convenience

GPIO.setwarnings(False)     # suppress warning message
GPIO.setmode(GPIO.BCM)      # use BCM labeling
                              # alternative is BOARD, by pin #
GPIO.setup(21,GPIO.OUT)      # declare pin as output

GPIO.output(21,GPIO.HIGH)    # set pin high
GPIO.output(21,GPIO.LOW)    # set pin low
```

GPIO.LOW and GPIO.HIGH just map to integers 0 and 1, actually

See <https://sourceforge.net/p/raspberry-gpio-python/wiki/BasicUsage/> for more

# Lab 7b

- Purpose: send data to DAC from Pi
  - ultimately, generate creative/custom waveform
    - i.e., something a standard function generator can't do
- Lab 7b nominally Thanksgiving week
  - but may wish to do early; just keep going after 7a
  - single write-up due Dec. 4

# Tips for Lab 7b

- Helps a lot to use sequential BCM numbers
  - allows simple `range ( )` loop to increment
  - makes coding compact, efficient, easy to modify
  - can also send list values to write all at once (later step)
- Determining bit values in integer
  - assume LSB (least significant bit) at `bcm_low`
  - `bitval = (intval >> (bcm_num - bcm_low)) & 0x01`
    - `bcm_num` loops through BCM GPIO numbers
    - right shift appropriate number of bits then mask LSB

# Lab 7b, continued

- After initial static outputs (to check behavior), go dynamic
- Initially, just a ramp
  - integer increments 0 to 255; back to 0 and on and on
    - shortcut: `intval += 1` (same as `intval = intval + 1`)
    - then check if `> 255` and reset to 0 if so
  - can nest inside: `while True:` for indefinite repeat
    - ctrl-C to terminate
  - at first, will be ratty and spiky due to non-simultaneous bit changes
    - will explore bit order and also list-write
    - then will filter out spikes